

z. 25.10, o. 118

Dane:

$$U_p = 230V$$

$$P_p = 650W$$

$$U_y = 100V$$

a) $P = U \cdot I$

$$I = \frac{P}{U}$$

$$P = U \cdot \frac{P}{U}$$

$$P = \frac{U^2}{R} \cdot R$$

$$P \cdot R = U^2$$

$$R = \frac{U^2}{P}$$

$$R = \frac{U_p^2}{P_p} = \frac{U_y^2}{P_y}$$

$$\frac{U_p^2}{P_p} = \frac{U_y^2}{P_y} \quad | \cdot P_y P_p$$

$$U_p^2 P_y \approx U_y^2 P_p \quad | : U_p^2$$

$$P_y = \frac{U_y^2}{U_p^2} P_p$$

$$P_y = \frac{(100V)^2}{(230V)^2} \cdot 650W = \frac{10000V^2}{52900V^2} \cdot 650W \approx 0,189 \cdot 650W \approx \underline{123W}$$

b) $I_y U_y = P_y$

$$I_y U_y = \frac{U_y^2}{U_p^2} P_p$$

$$I_y = \frac{U_y}{U_p^2} P_p$$

$$I_y = \frac{I_{0,y}}{\sqrt{2}} \cdot \sqrt{2}$$

$$I_y \sqrt{2} = I_{0,y}$$

$$I_{0,y} = \frac{U_y}{U_p^2} P_p \sqrt{2}$$

$$I_{0,y} = \frac{U_y P_p \sqrt{2}}{U_p^2}$$

$$I_{0,y} = \frac{100V \cdot 650W \cdot \sqrt{2}}{2 \cdot (230V)^2} \approx \underline{1,74A}$$

c) $E = P_p t_p$

$$E = P_y t_y$$

$$P_y t_y = P_p t_p \quad | : P_y t_p$$

$$\frac{t_y}{t_p} = \frac{P_p}{P_y}$$

$$\frac{t_y}{t_p} = \frac{P_p}{\frac{U_y^2}{U_p^2} P_p}$$

$$\frac{t_y}{t_p} = \frac{U_p^2}{U_y^2}$$

$$\frac{t_y}{t_p} = \frac{(230V)^2}{(100V)^2} \approx 5$$

Odp.: W Japonii zapotrawienie wody będzie trwało około 5 razy dłużej.